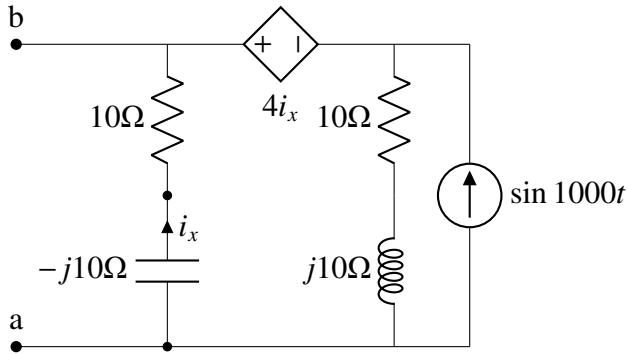



GATE: 51.2023

EE22BTECH11005- Ambati Krishna Kaustubh*

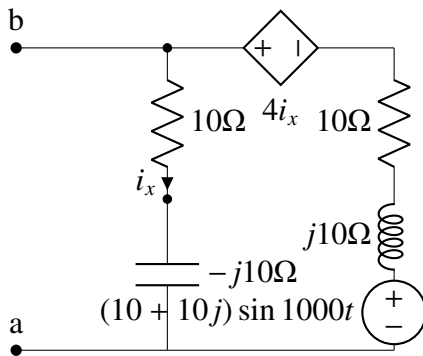Question: For the circuit shown, if $i = \sin 1000t$, the instantaneous value of the Thevenin's voltage (in volts) across the terminals a and b at time $t = 5\text{ms}$ is



Solution: By source transforming the given circuit we get



Applying KVL in the loop,

$$10 + j10 + 4i_x - (j10 + 10 + 10 - j10)i_x = 0 \quad (1)$$

$$10 + j10 + 4i_x - 20i_x = 0 \quad (2)$$

$$i_x = 0.884 \angle 45^\circ \quad (3)$$

$$V_{th} = i_x(10 - j10) \quad (4)$$

$$= 12.5 \angle 0^\circ \quad (5)$$

$$V_{th} = 12.5 \sin 1000t \quad (6)$$

$$t = 5\text{ms} \quad (7)$$

$$\therefore V_{th} = -11.985\text{V}$$